

# Evaluation of Design Trade-offs for Adders in Approximate Datapath


Kan Shi and George A. Constantinides  
EEE Department, Imperial College London

February 19, 2015

WAPCO'15 Amsterdam, Netherland

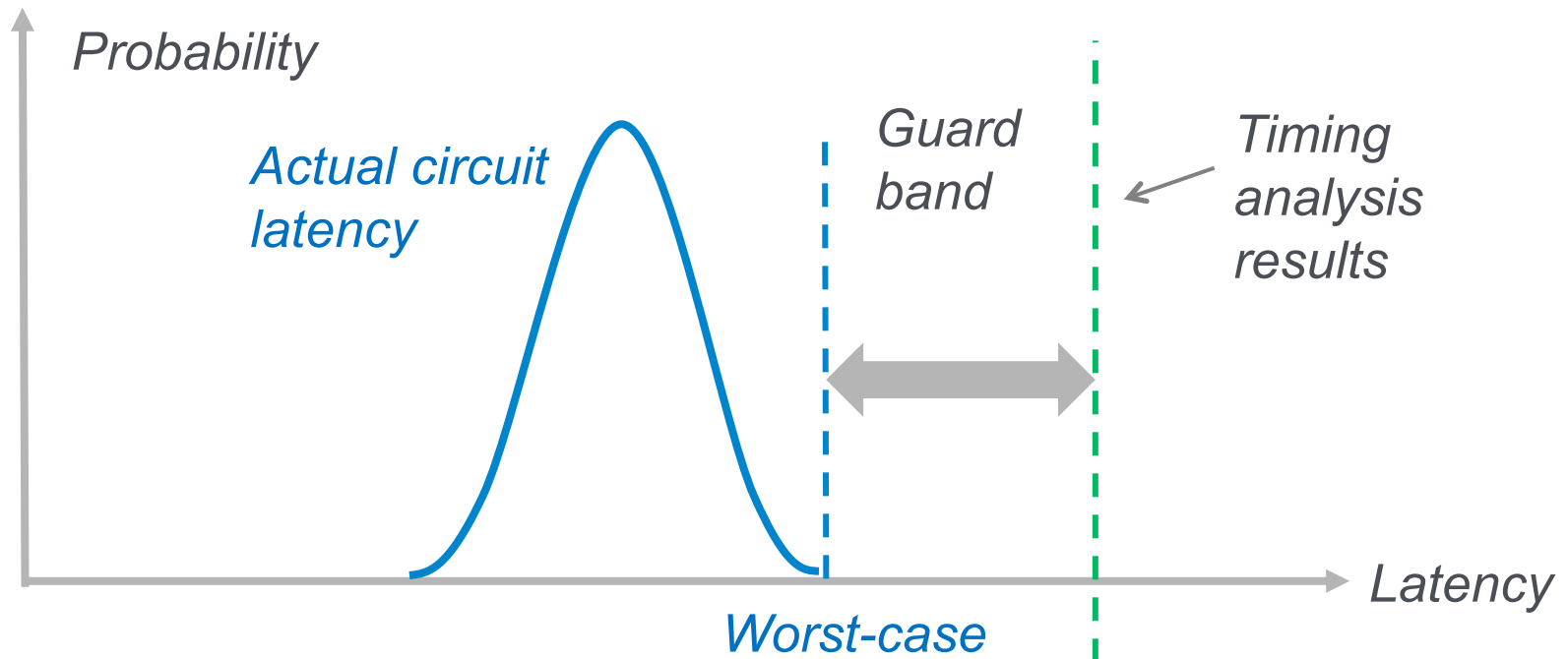
# It is all about Performance

- Digital circuits are designed to ensure timing closure



 
# It is all about Performance

- Digital circuits are designed to ensure timing closure
- Designing for worst cases is Expensive
  - STA is conservative





# Worst Case?

 

# Worst Case?


- Cost +

  

- Accuracy Requirement +


# Our Vision: Design Scenarios

(FCCM'13, ISCAS'13, TRETS'14)

 

# Our Vision: Design Scenarios


(FCCM'13, ISCAS'13, TRETS'14)

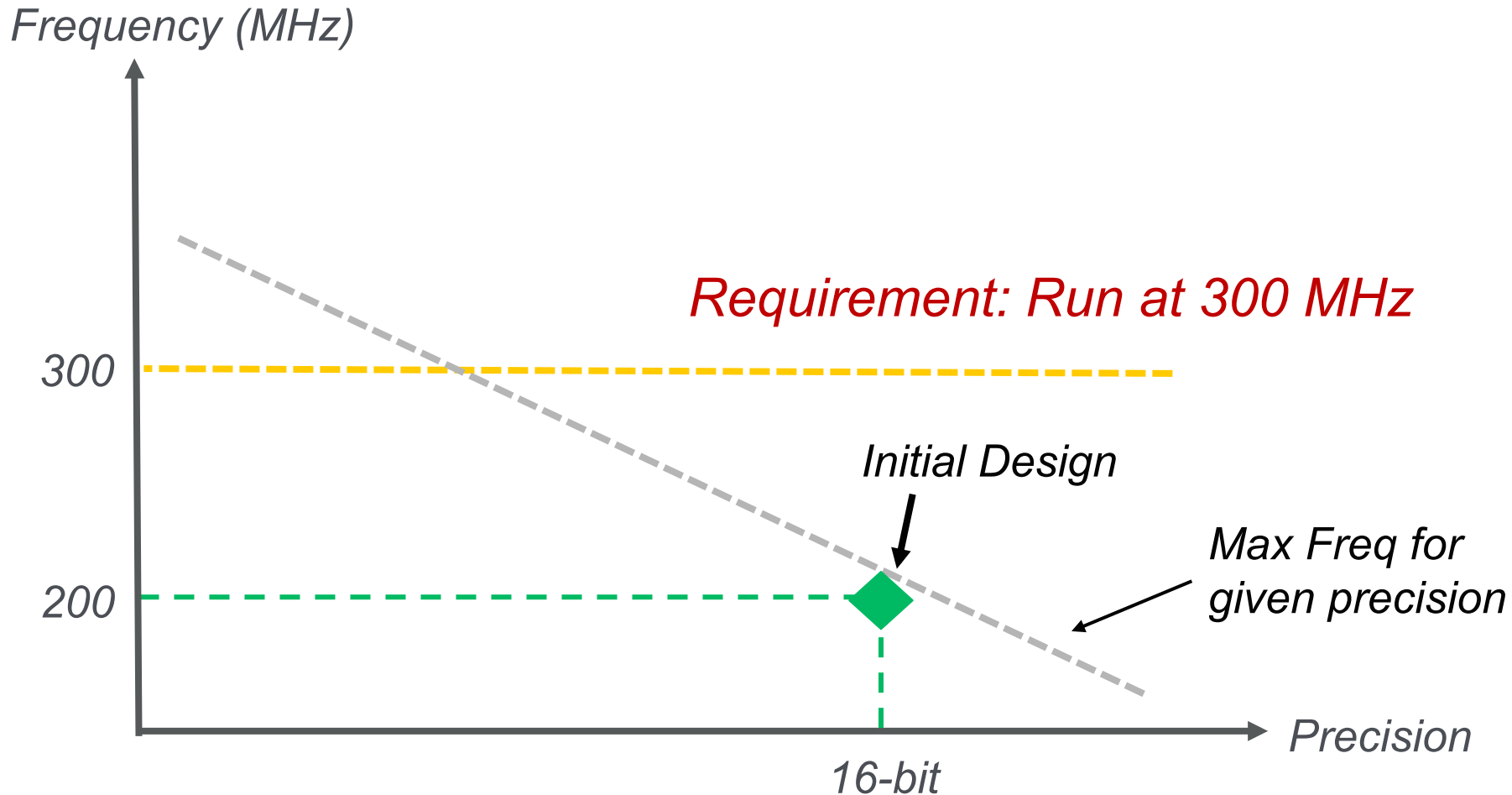



# Our Vision: Design Scenarios


(FCCM'13, ISCAS'13, TRETTS'14)

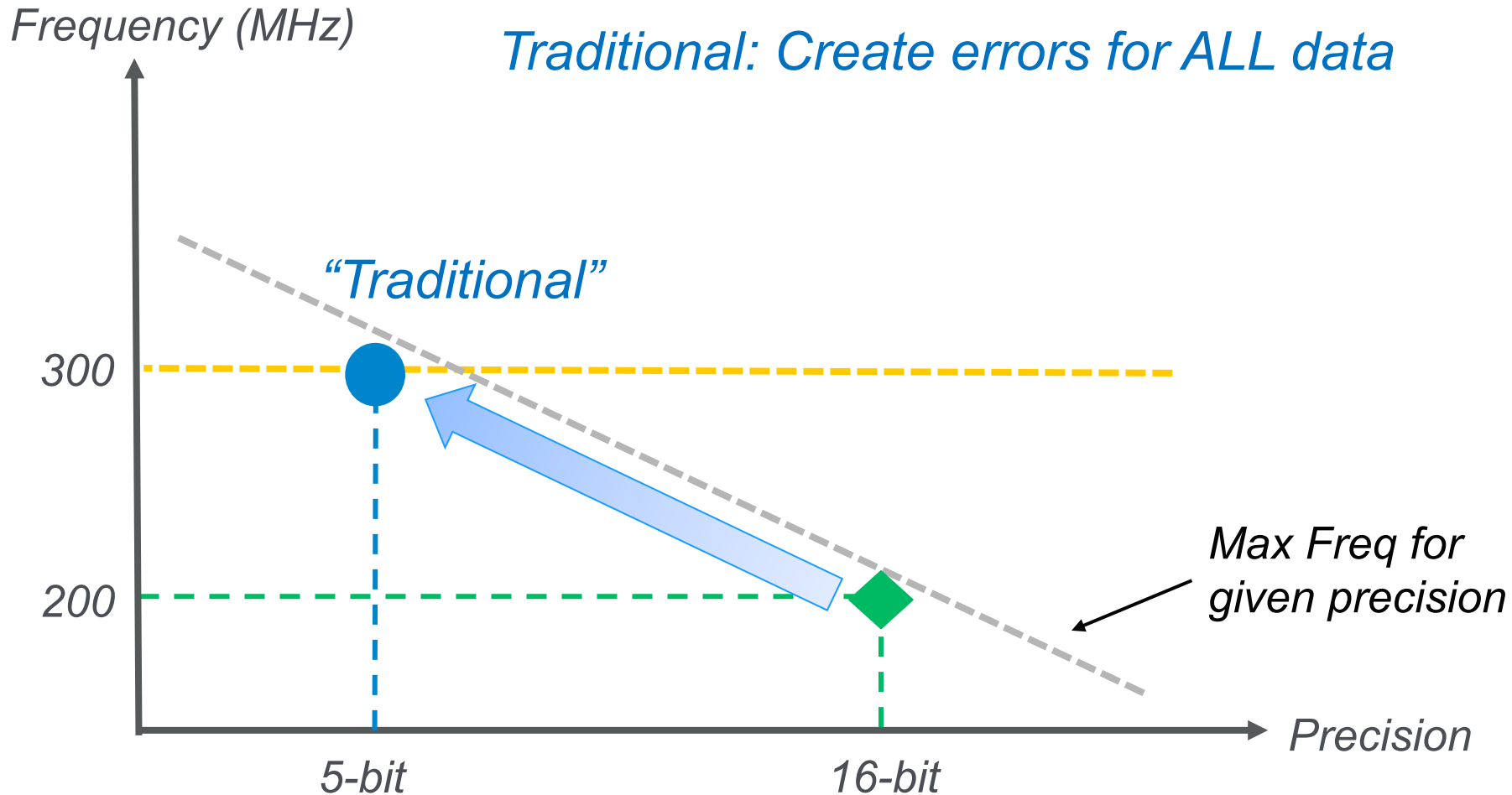



# Our Vision: Design Scenarios

(FCCM'13, ISCAS'13, TRETS'14)

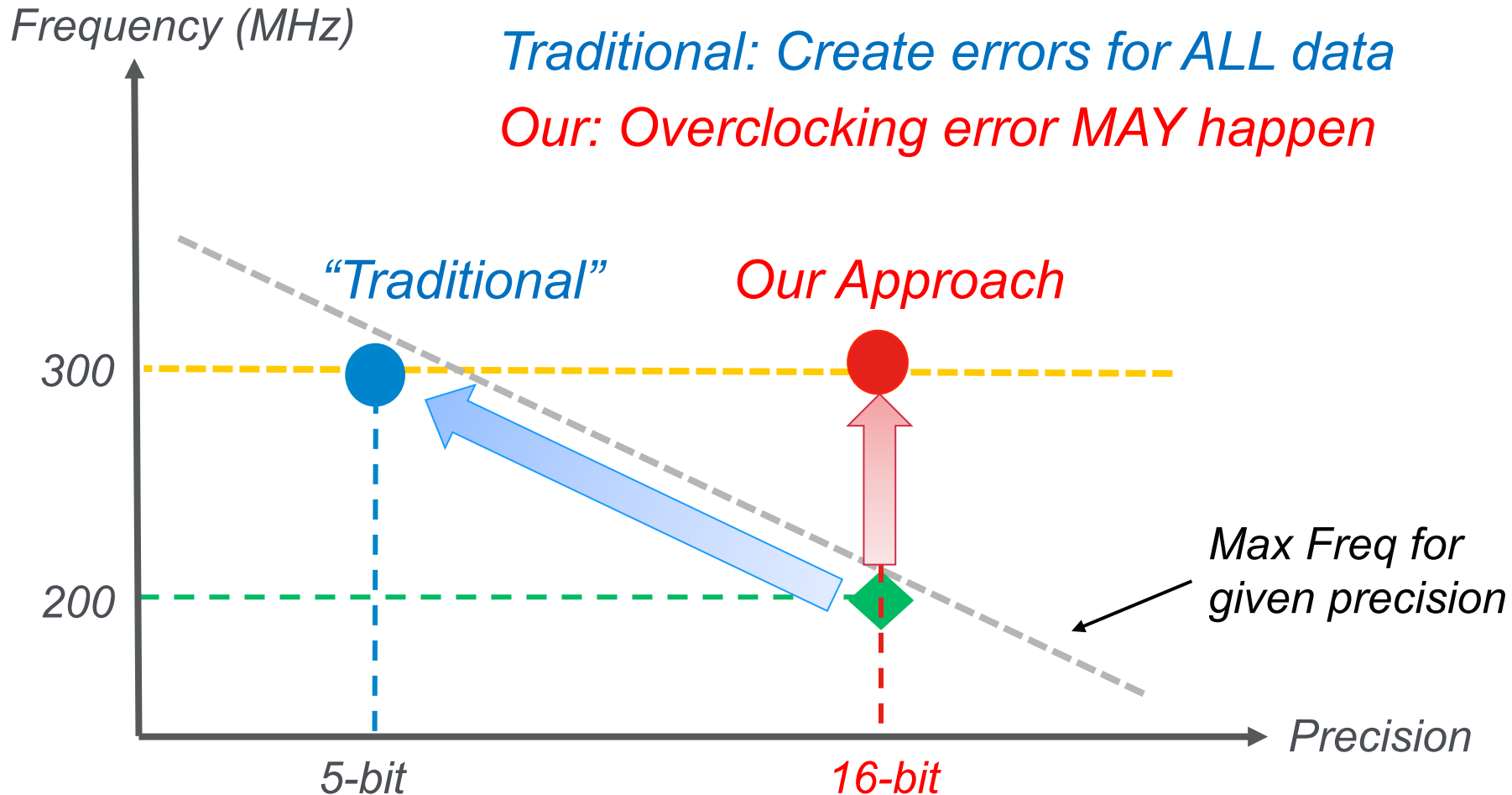

# Our Vision: Different Computer Arithmetic

*(DAC'14, ICFPT'14)*

- “Online Arithmetic” is MSB-first arithmetic
  - All I/Os are processed in the MSB-first manner
- Online Arithmetic is “overclocking friendly”
  - Overclocking errors only occur at LSBs.

# Our Vision: Different Computer Arithmetic

(DAC'14, ICFPT'14)

- “Online Arithmetic” is MSB-first arithmetic
  - All I/Os are processed in the MSB-first manner
- Online Arithmetic is “overclocking friendly”
  - Overclocking errors only occur at LSBs.

*Example: Image Filter (DAC'14), 25% Speed-up*



*Traditional  
Arithmetic*

*SNR=9dB*



*Online  
Arithmetic*

*SNR=36.2dB*

# Our Contributions: This Paper

- Detailed evaluation of three adder structures:
  - Ripple carry adder
  - Carry select adder
  - Online arithmetic adder
- Optimum design choice under accuracy, performance and area trade-offs


# Outline

---

- Motivation
- **Background**
  - **Adders with conventional arithmetic**
  - **Online arithmetic**
- Design trade-offs for adders
- Evaluation of the optimum adder design choice
- Conclusion

 
# Adders with Conventional Arithmetic

- Ripple carry adder
  - Frequency determines max carry propagation length


 
# Adders with Conventional Arithmetic

- Ripple carry adder
  - Frequency determines max carry propagation length




- Two design scenarios: truncation or overclocking (see paper)



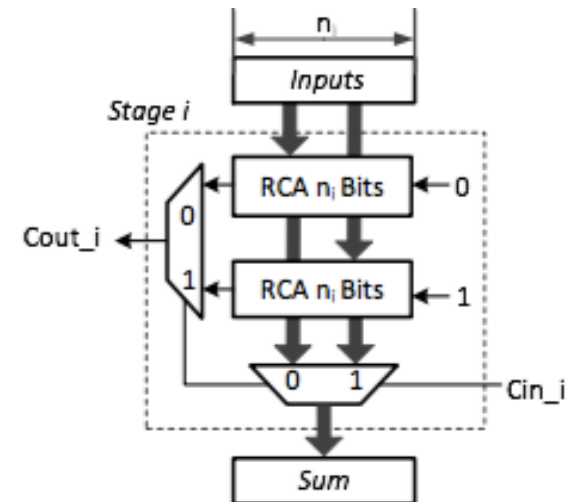
# Adders with Conventional Arithmetic

- Ripple carry adder
  - Frequency determines max carry propagation length
  - Two design scenarios: truncation or overclocking (see paper)
- Carry select adder
  - Use more area for high performance
  - Evaluate its truncation scenario
  - Details please see paper


 
# Online Arithmetic: Background

- What is it?
  - Online Arithmetic performs computation in an **MSD-first manner**.
  - It is initially designed for digit-serial operation.




# Online Arithmetic: Background

- What is it?
  - Online Arithmetic performs computation in an **MSD-first manner**.
  - It is initially designed for digit-serial operation.
- How is this possible?
  - Requires a flexibility in computing outputs **only based on partial information** of inputs.
  - Redundancy in the number representation.
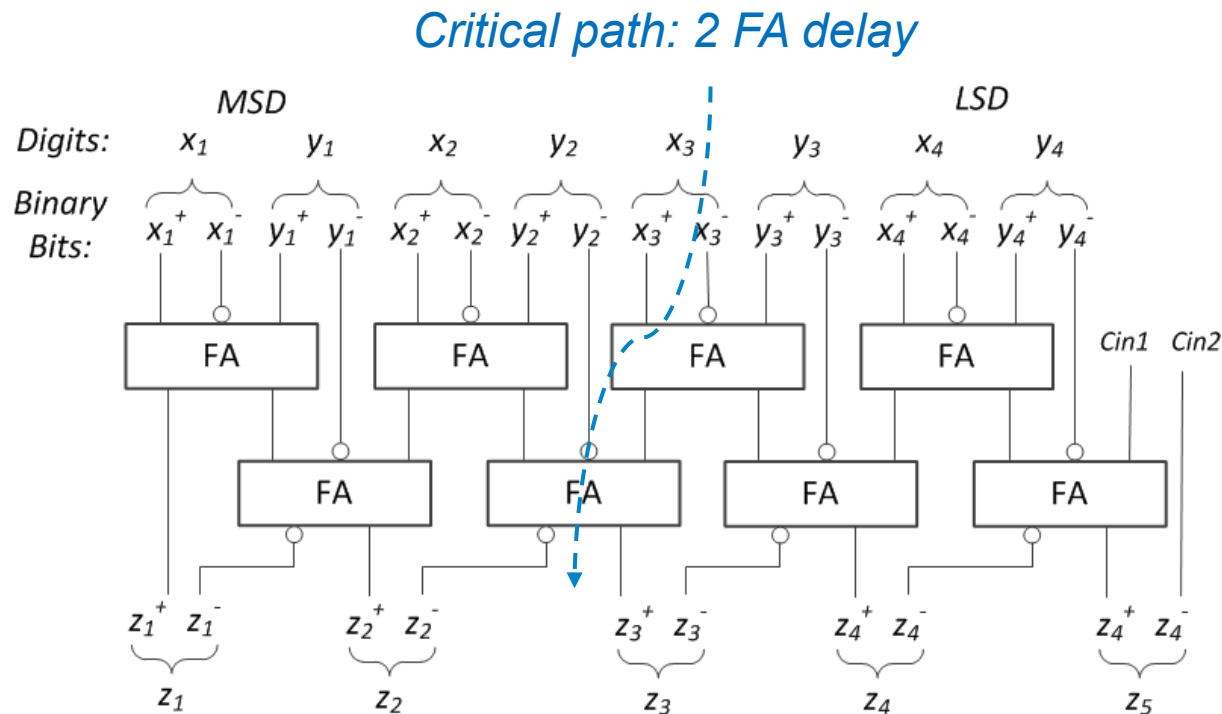
# Online Arithmetic: Adder

- Features:
  - Binary, digit parallel
  - Fast: critical path is irrelevant to operand precision




# Outline

---

- Motivation
- Background
- **Design trade-offs for adders**
  - **Accuracy, performance and area**
- Evaluation of the optimum adder design choice
- Conclusion

# Design Trade-offs: Accuracy vs Frequency

- Original word-length = 32 bits

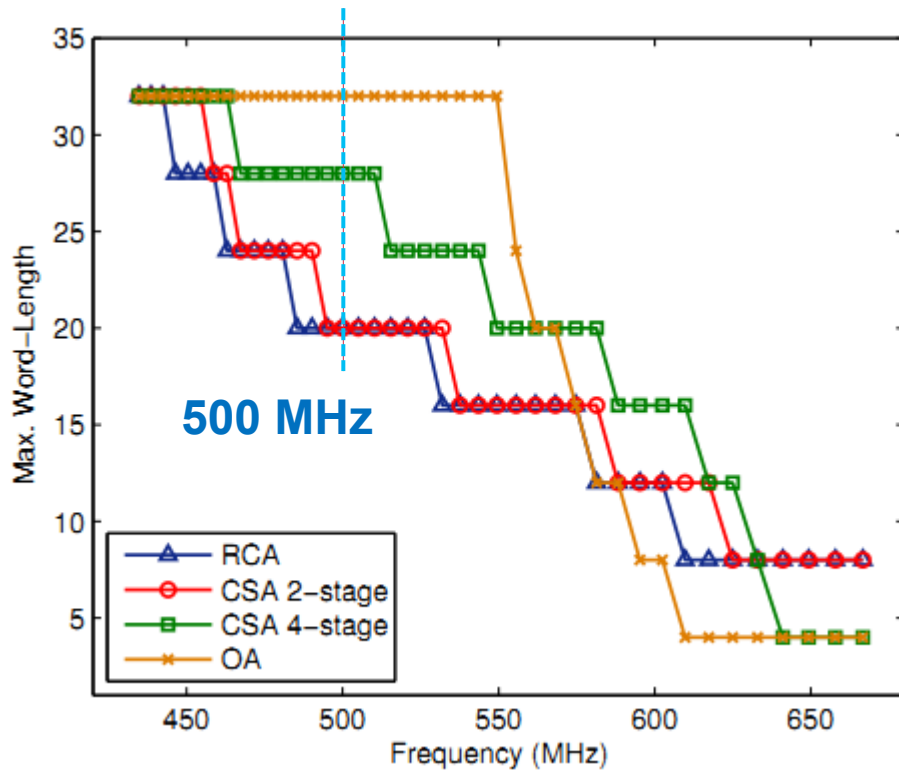


Max. Word-length

| Freq (MHz) | RCA | CSA-2 | CSA-4 | Online Adder |
|------------|-----|-------|-------|--------------|
| 500        | 20  | 20    | 28    | 32           |
|            |     |       |       |              |
|            |     |       |       |              |

# Design Trade-offs: Accuracy vs Frequency

- Original word-length = 32 bits

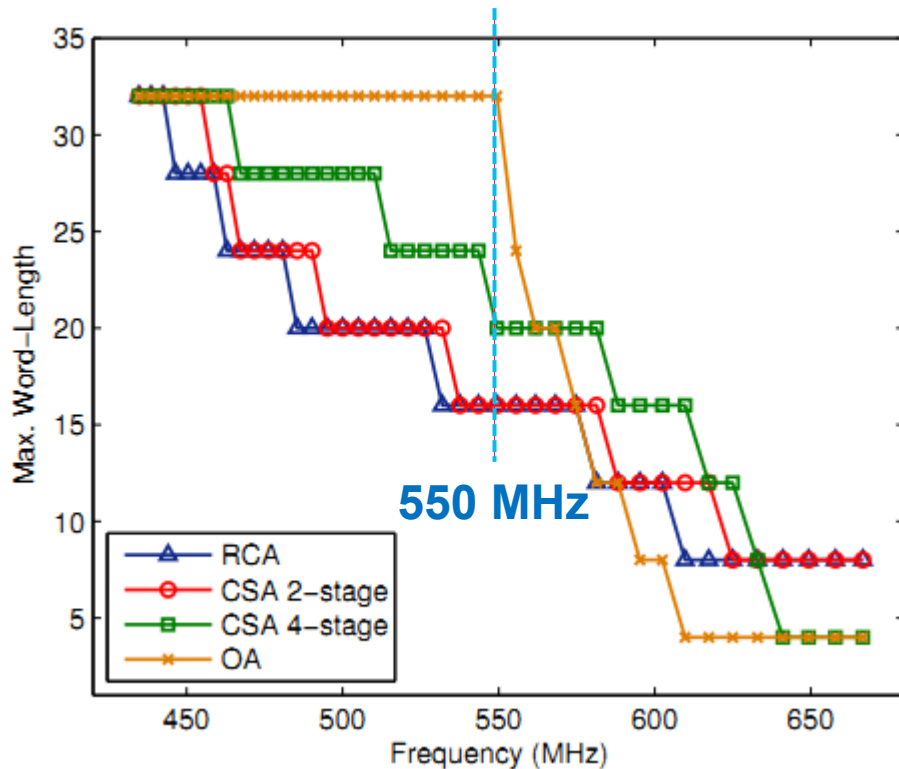

## Max. Word-length


| Freq (MHz) | RCA | CSA-2 | CSA-4 | Online Adder |
|------------|-----|-------|-------|--------------|
| 500        | 20  | 20    | 28    | 32           |
| 550        | 16  | 16    | 20    | 32           |
|            |     |       |       |              |

CSA and OA are designed to run faster than RCA



# Design Trade-offs: Accuracy vs Frequency

- Original word-length = 32 bits

 


Max. Word-length

| Freq (MHz) | RCA | CSA-2 | CSA-4 | Online Adder |
|------------|-----|-------|-------|--------------|
| 500        | 20  | 20    | 28    | 32           |
| 550        | 16  | 16    | 20    | 32           |
| 600        | 12  | 12    | 16    | 8            |

# Design Trade-offs: Area vs Frequency

Area vs Frequency

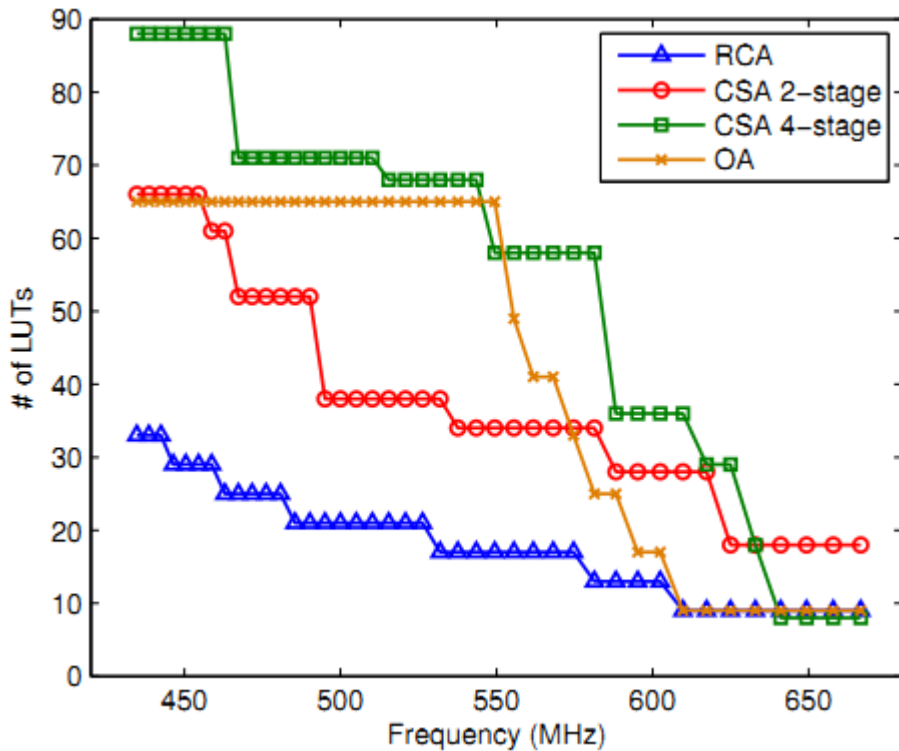

Area Overhead than RCA

| Freq (MHz) | CSA-2 | CSA-4 | Online Adder |
|------------|-------|-------|--------------|
| 500        | 1.8x  | 3.4x  | 3.1x         |
| 550        | 2.0x  | 3.4x  | 3.8x         |
| 600        | 2.2x  | 2.8x  | 1.3x         |


# Outline

---

- Motivation
- Background
- Design trade-offs for adders
- **Evaluation of the optimum adder design choice**
  - **Example: limited area budget**
  - **Results with a variety of area constraints**
- Conclusion


 
# Design Trade-offs: Limited Area Budget

- Optimal design achieves **minimum error**
- Available LUT = 35: RCA with overclocking



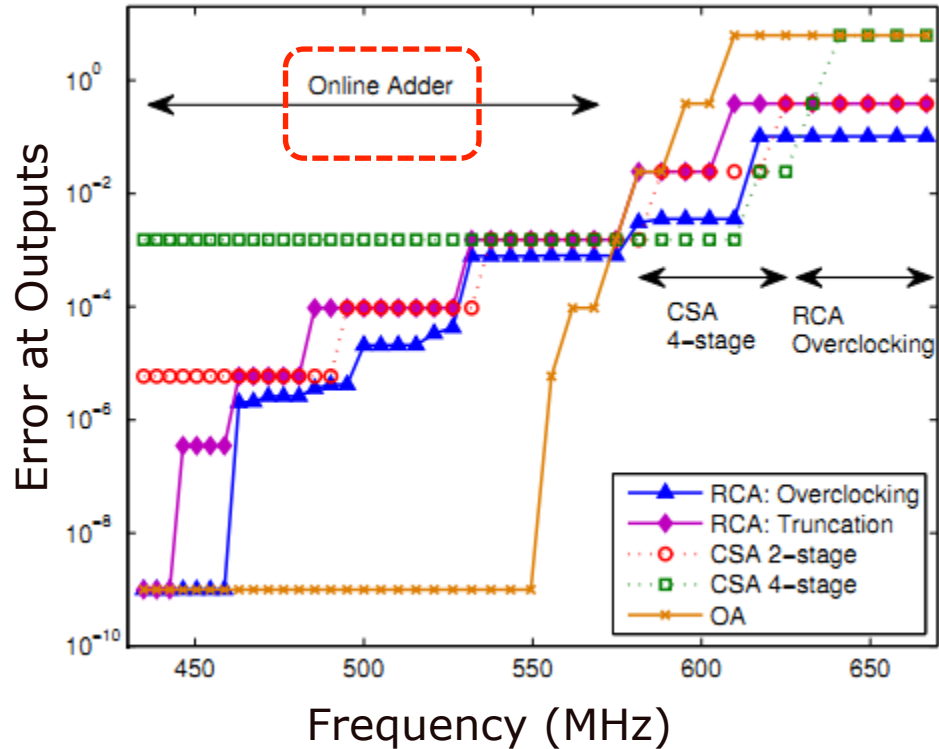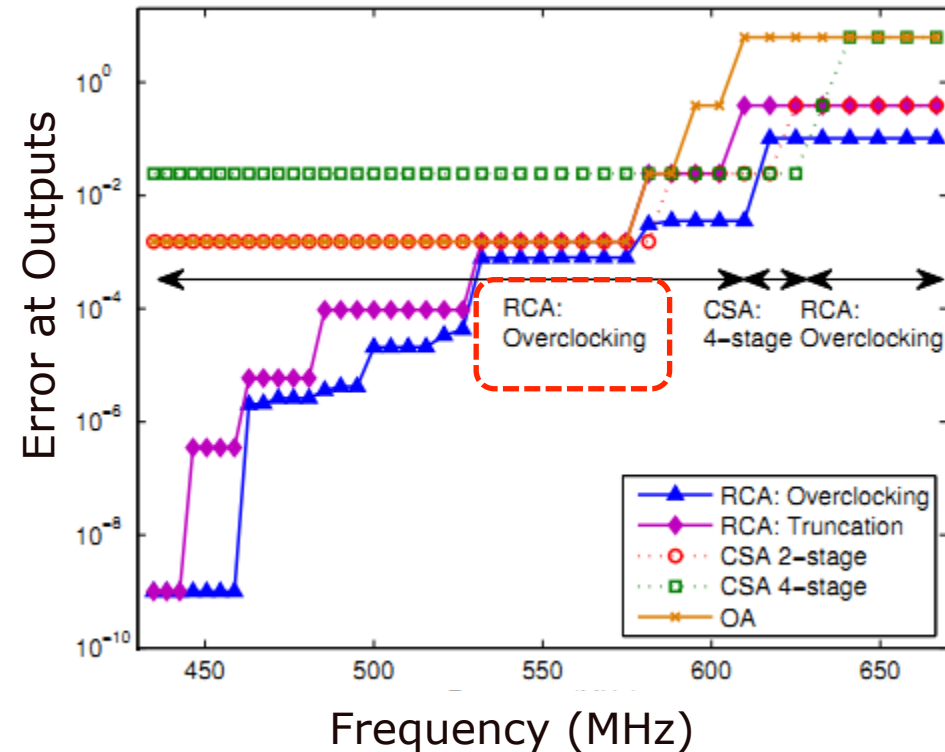
# Design Trade-offs: Limited Area Budget

- Optimal design achieves **minimum error**
- Available LUT = 35: RCA with overclocking
- Available LUT = 55: Online adder



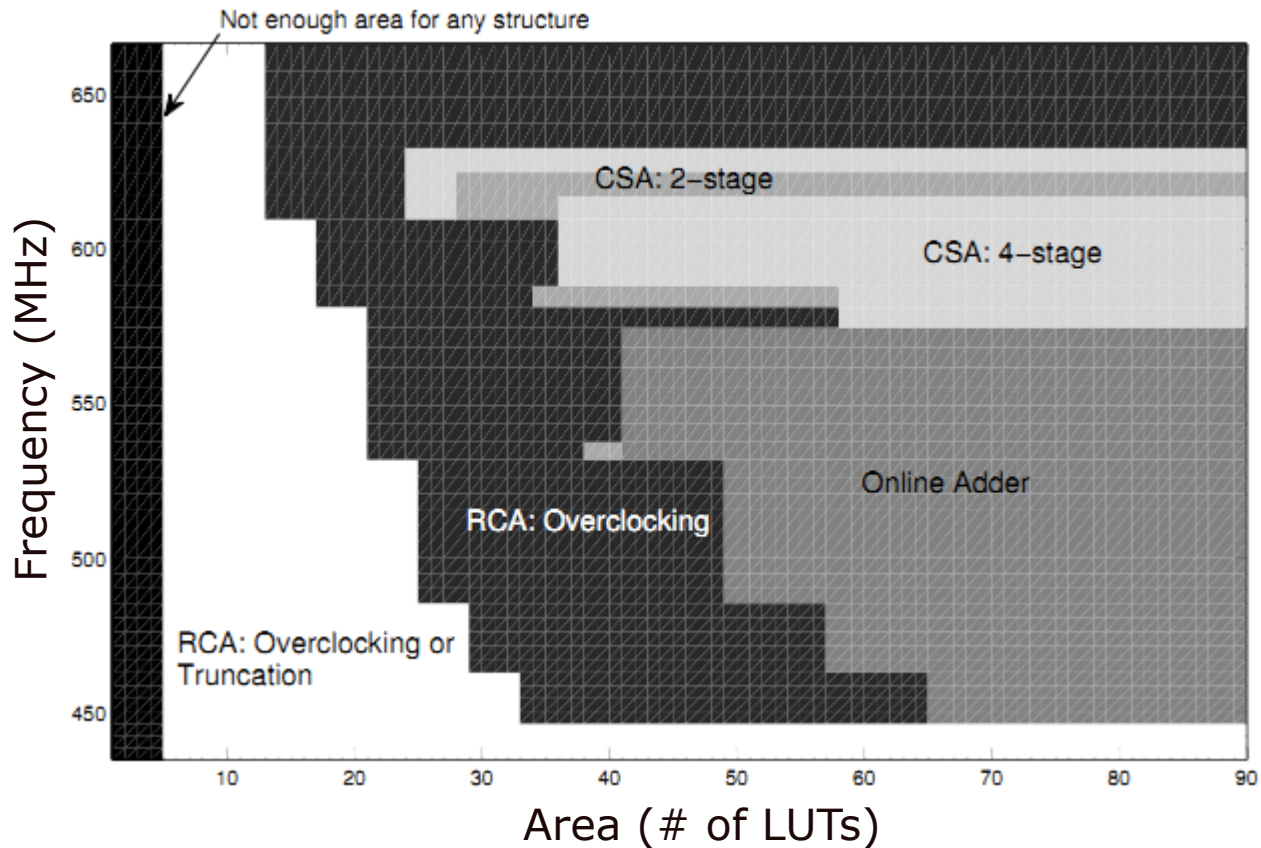
# Optimum Adder Design Choice

- Optimal design achieves **minimum error**


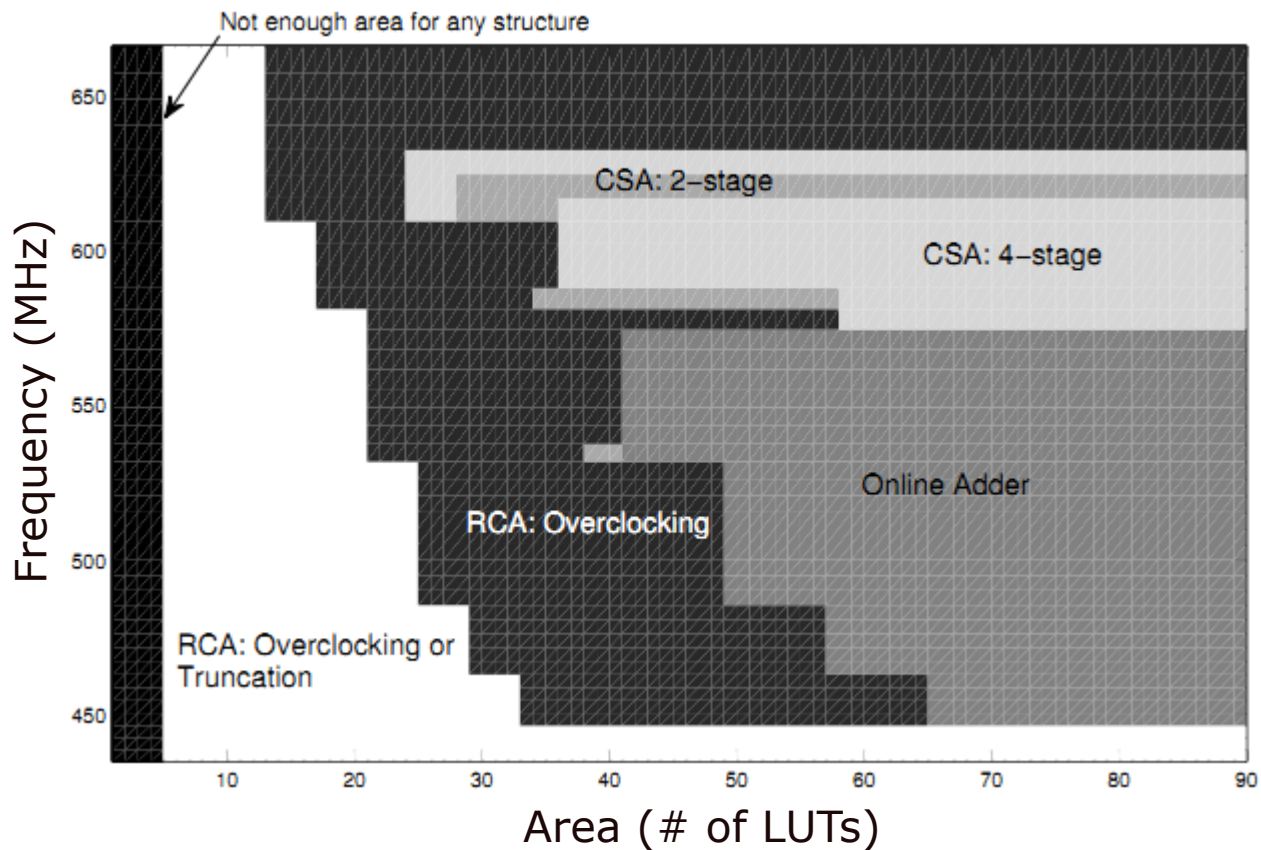
# Optimum Adder Design Choice

- Optimal design achieves minimum error
- Optimal design achieves **fastest frequency**: see paper






# Conclusion

- We evaluated 3 adder structures: ripple carry adder, carry-select adder and online adder
- We considered 2 design scenarios that trade accuracy for performance: overclocking and truncation
- We show that
  - Limited area budget: using RCA with overclocking
  - Relaxed area budget: using online adder
- Details in papers and poster


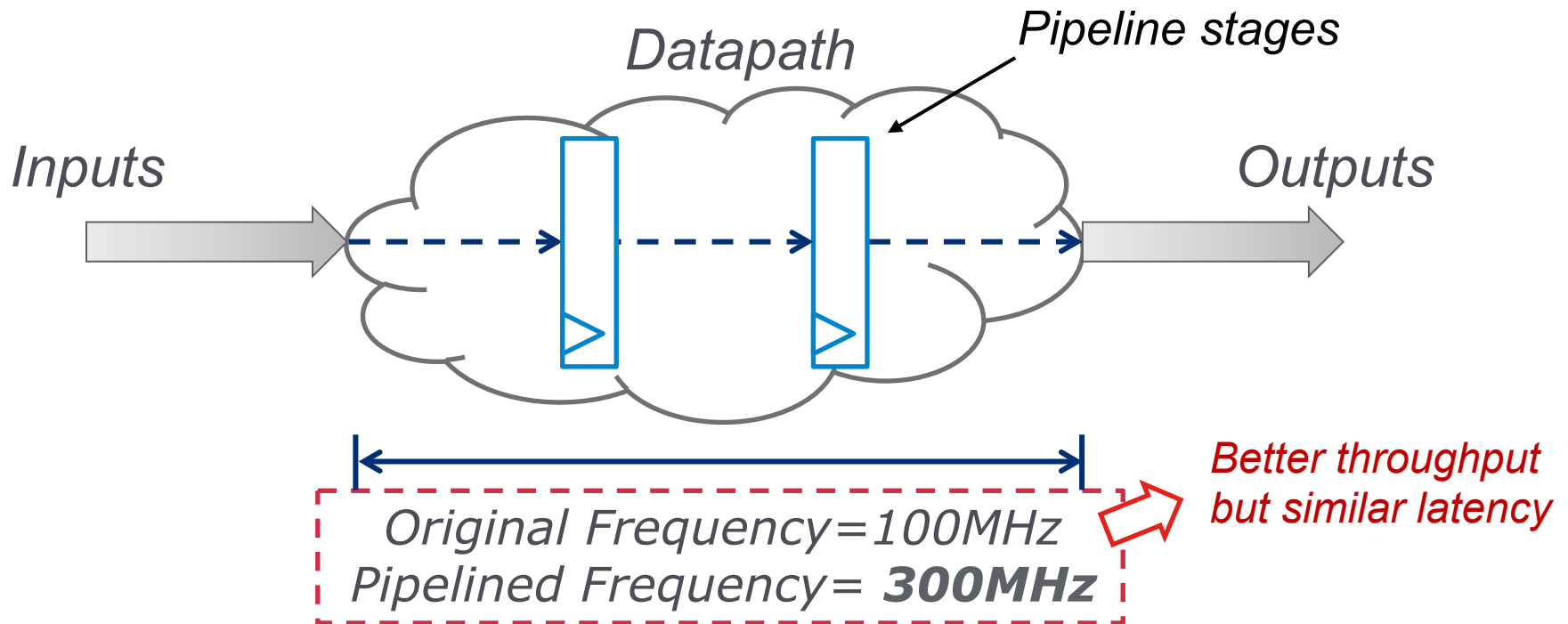
# It is all about Performance

- FPGAs run at much lower frequency than CPUs and GPUs
  - Pipelining? : not helpful in reducing datapath latency



# It is all about Performance--backup

- FPGAs run at much lower frequency than CPUs and GPUs
  - Pipelining? : not helpful in reducing datapath latency
- EDA tools provide conservative timing to cover variations

